

APRIL/MAY 2018

**MPH14A — ELECTRONIC DEVICES AND  
APPLICATIONS**

Time : Three hours

Maximum : 75 marks

SECTION A — (5 × 6 = 30 marks)

Answer ALL the questions.

1. (a) Explain the fabrication of voltage regulators by using monolithic technology.

Or

- (b) Write short notes on integrated circuit multipliers.

2. (a) What is a PIN diode? Discuss its characteristics.

Or

- (b) What is a photo transistor? Explain its action and discuss its features.

3. (a) Construct a Schmitt trigger circuit using IC 555 and describe its working.

Or

- (b) What is PLL? Design a PLL with IC 555 timer and explain its working.

1375

4. (a) Construct a logarithmic amplifier circuit with an op-amp and describe its operation.

Or

- (b) With a neat circuit diagram with op-amp, explain the working of a sine wave generator.

5. (a) Describe the generation and demodulation of pulse position modulation.

Or

- (b) Explain the different modes of modem operations.

SECTION B — (3 × 15 = 45 marks)

Answer any THREE questions.

6. Write short notes on the logic families
- (a) Schottky TTL
  - (b) P & N MOS and
  - (c) tristate
7. (a) Draw the Pin out diagram of a seven segment display and explain its working.
- (b) Write short notes on IR and UV detectors.

8. With a neat diagram, give a complete description about IC 565 and describe its lock in range and capture range.

9. Using op-amps construct the following circuits and explain their actions.

- (a) Schmitt trigger
- (b) Astable and monostable multivibrators.

10. (a) Explain the principles of PCM.
- (b) Describe the generation and demodulation of PCM.