



APRIL/MAY 2019

MPH14A — ELECTRONIC DEVICES AND
APPLICATIONS

Time : Three hours

Maximum : 75 marks

SECTION A — (5 × 6 = 30 marks)

Answer ALL questions.

1. (a) With a circuit diagram explain tri state logic circuits.

Or

- (b) With a circuit diagram explain how pressure transducer is fabricated by integrated circuit.

2. (a) With a block diagram explain the working of NE/SE 566 voltage controlled oscillator

Or

- (b) Derive the expression for capture range of PLL IC 565.

3. (a) Explain the construction and characteristics of LDR.

Or

- (b) Write short notes on IR detector.

4. (a) Explain the operation of monostable multivibrator using Op-Amp with circuit diagram.

Or

- (b) Explain the working of non-inverting Schmitt trigger using Op-Amp with circuit diagram.

5. (a) Explain the PWM technique and state its advantages.

Or

- (b) Describe the MODEM RS-232 interfacing.

SECTION B — (3 × 15 = 45 marks)

Answer any THREE questions.

6. (a) With a circuit diagram describe the various steps to fabricate MOSFET from Si wafer.
(b) Discuss briefly fabrication of Schottky transistor.
7. Describe the working of a solar cell along with its characteristics and hence derive an expression for the efficiency of a solar cell.
8. With a circuit diagram explain the working of IC 555 as a monostable multivibrator and hence derive the expression for the pulse width of it.

9. (a) Draw the circuit diagram of a second order Butterworth active low pass filter and derive an expression for its transfer function.

- (b) With a circuit diagram explain the working of log amplifier.

10. Give the principle of pulse code modulation. Explain the generation and demodulation of pulse code modulation.

